



Cross Coupled Oscillator Design

First Pass

1) $P_{DC} = 1mW$, $V_{DD} = 1V$, $V_{Th} = 580mV$, $\theta_L = 8$, $C_{out} = 20fF$.

2) $I_{ss} = \frac{P_{DC}}{V_{DD}} = \underline{1mA}$;

$$R_p = \frac{\pi V_{DD} V_{Th}}{4 P_{DC}} = \frac{\pi \times 0.58}{4 \times 10^{-3}} = \underline{455\Omega}$$

3) $L_1 = \frac{R_p}{\theta_L \omega_0} = \frac{455}{8 \times 2\pi \times 10^{10}} = \underline{0.905\text{ nH}}$

$$C_1 = \frac{1}{\omega_0^2 L_1} = \frac{280fF}{\underbrace{10fF}_{C_{out}}} = \underline{27fF}$$


4) $\frac{W}{L} = \underline{5\mu m}$ with 10 fingers.

Effect of Tail Current


$$\overline{i_n^2} = \overline{i_n^2}_{\text{flicker}} + \overline{i_n^2}_{\text{white}}$$

↓ ↓

how freq.
($\ll f_0$) Wideband.

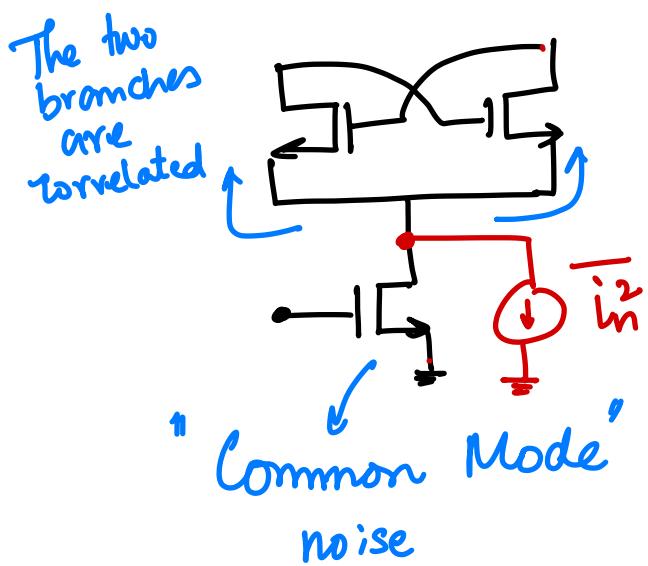

Phase Noise

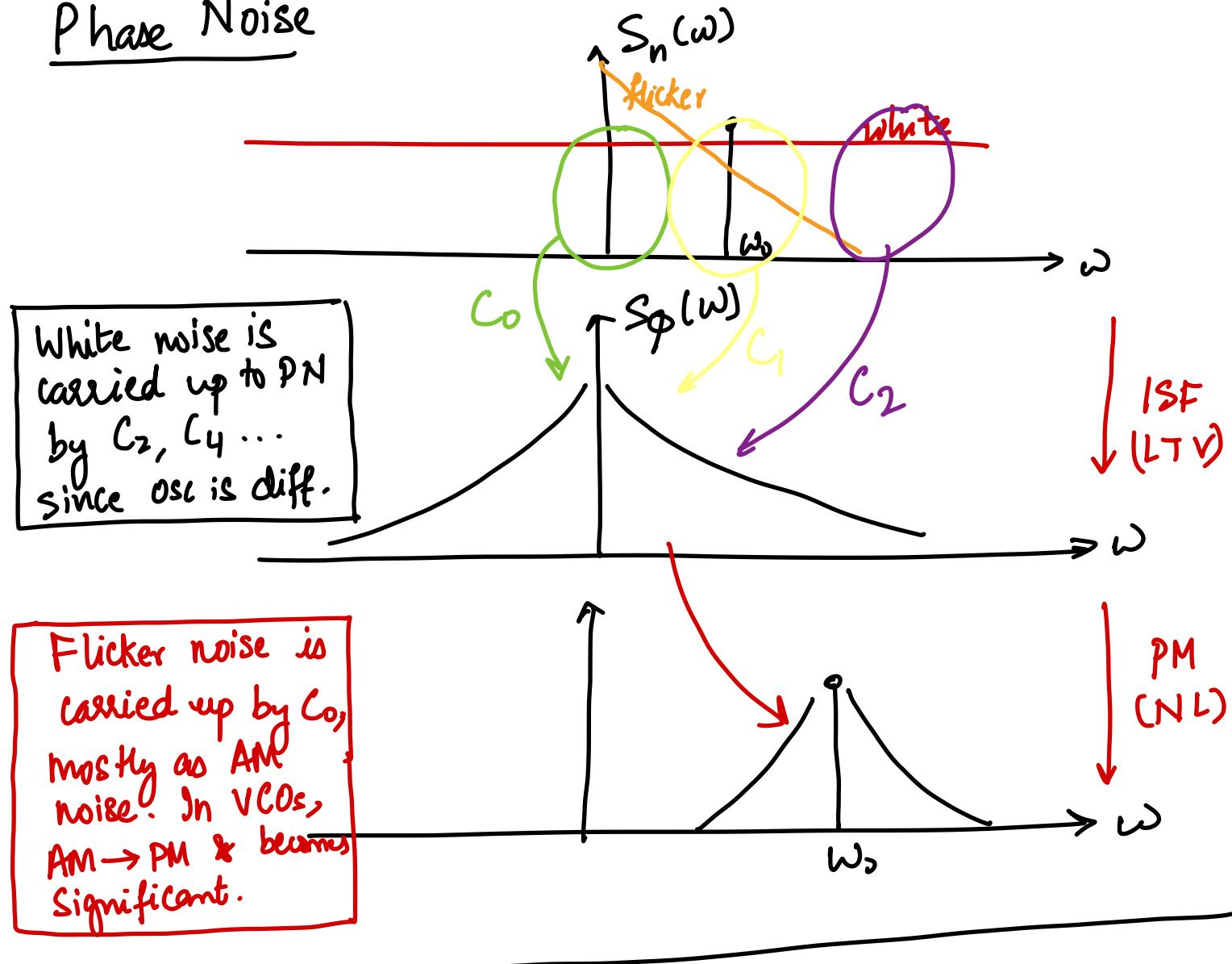


Current mirror

$$I_D = \frac{\left(\frac{W}{L}\right)_3}{\left(\frac{W}{L}\right)_4} \cdot \frac{1 + \lambda V_{DS_3}}{1 + \lambda V_{DS_4}} \cdot I_{SS}$$

CLM coeff.

Significant when $L \rightarrow \min.$

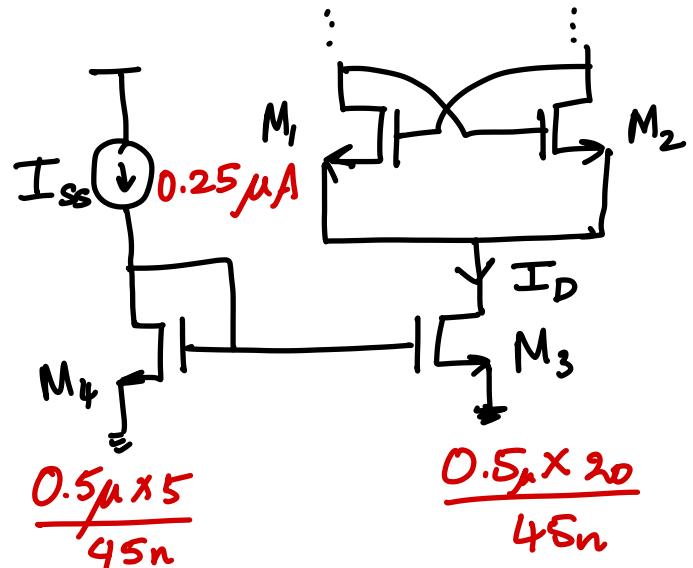

(Flicker)

Noise: Noise of M_4 is amplified by the current mirror's gain.

Suppressing the Flicker Noise of M4

$$S_f(f) = \frac{K}{C_{ox}} \frac{1}{WL} \frac{1}{f} \quad \left. \right\} \text{Flicker Noise Spectrum.}$$

→ Larger area "averages out" the impact of Flicker noise.

